


# Lab 2 - Time Muxplexed dual Seven Segment display

18 available breadboard switches

- 4 additional DIP
- 7 segment controls
- 2 anode controls


\* LED Summage! display on 5 LEDs

3 by FPGA, 2 by MCU echo.

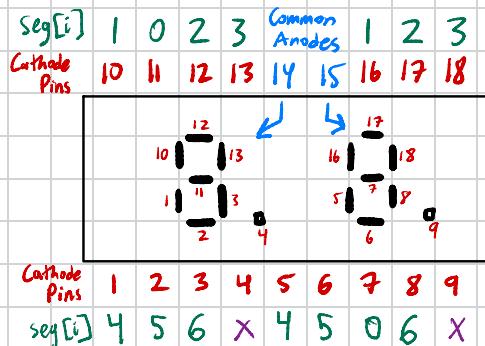

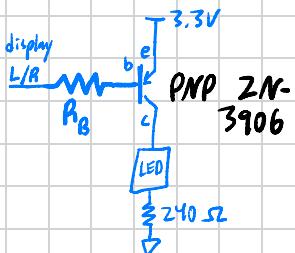
## Transistor Calculations

We use the following transistor circuit as a PNP transistor switch to send power to the LED segments:



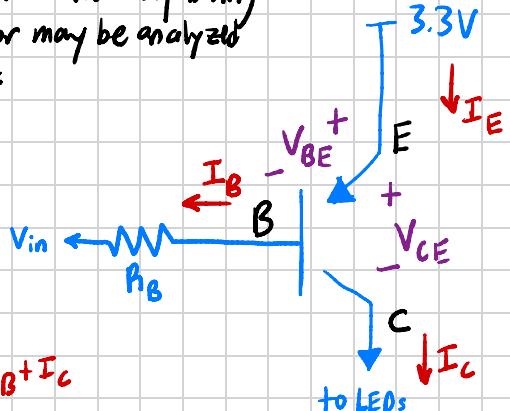The transistor and neighboring base resistor may be analyzed as follows:




$$I_E = I_B + I_C$$

$$I_C = \beta I_B = 10 I_B$$


$$R_B = \frac{V_{in} - V_{BE}}{I_B} = \frac{3.3 - 0.7}{I_B}$$

Let  $I_B = 6\text{mA}$  max.  
 $I_C = 60\text{mA}$ , enough to power every segment without ever exceeding 30mA each.

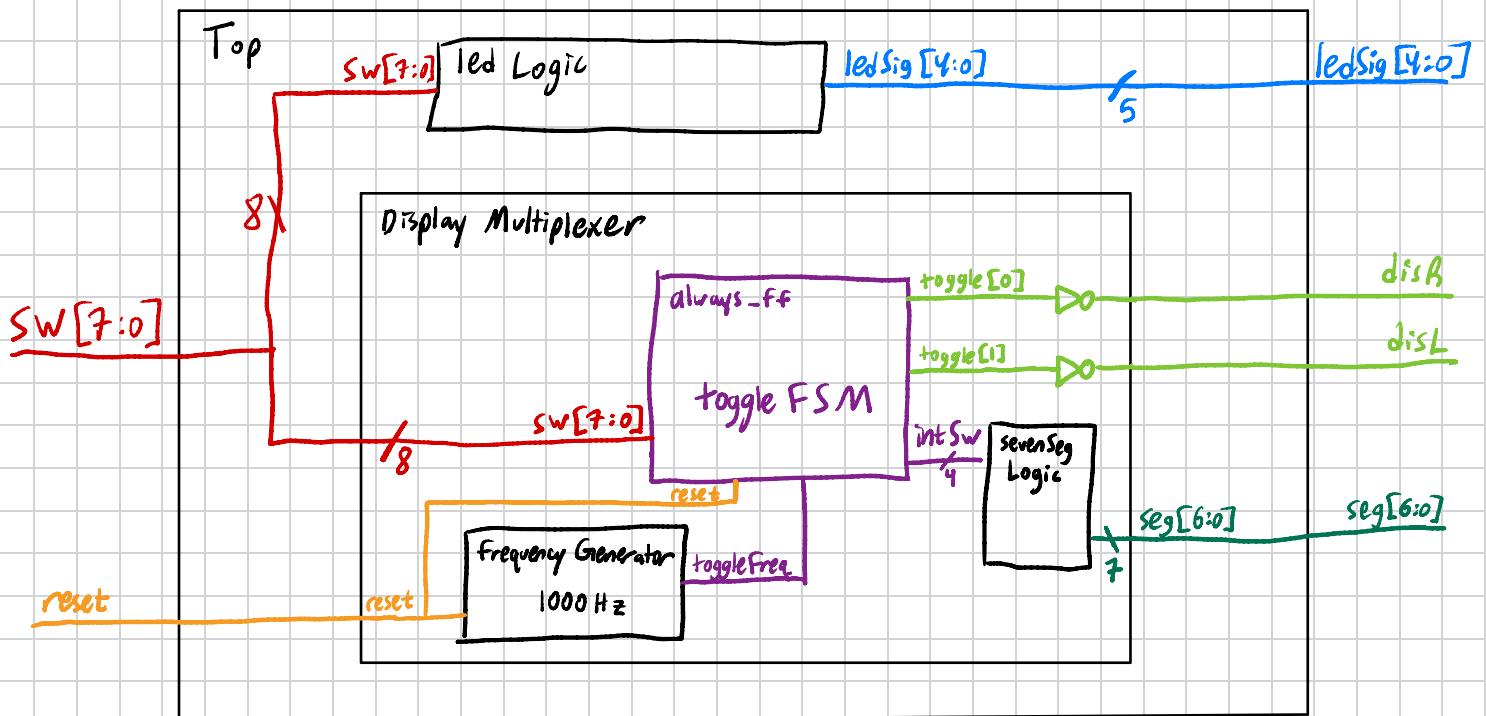Additionally, using 3.3V logic, our iCE40 FPGA chip recommends +/- 8mA as a current in/out limit on our GPIO pins. 6mA sits below this. Note: actual  $R_B = 470\Omega \rightarrow I_B = 5.5\text{mA}$ .



### Toggle FSM:

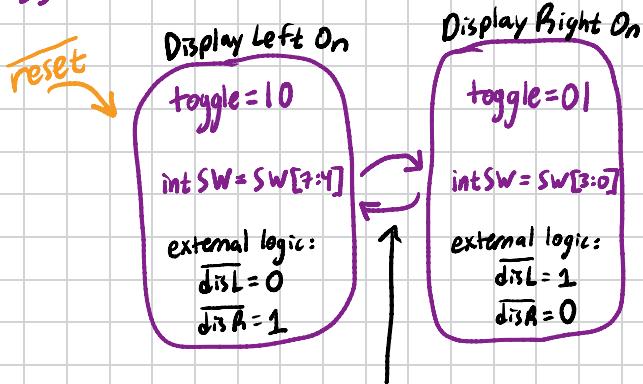

Triggered by toggleFreq at 1000Hz

'h02c7  
 $\text{var2} = 0000\ 0010\ 1100\ 0111$

110 100  
1011